

UNDERSTAND, DESCRIBE AND EXPLAIN:

To understand that common appliances run on electricity	<i>Electricity</i>	<i>Electric current</i>	<i>Flow</i>	<i>Electric charge</i>	<i>Generate</i>	<i>Current electricity</i>	<i>Material</i>	<i>Wires</i>
	<i>Power source</i>	<i>Appliance</i>	<i>Batteries (DC)</i>	<i>Mains electricity (AC)</i>	<i>Direct</i>	<i>Alternating</i>	<i>Energy source</i>	
	<i>Primary/secondary energy source</i>		<i>Fossil fuels</i>	<i>Wind power</i>	<i>Solar power</i>	<i>Hydro power</i>	<i>Renewable/Non-renewable</i>	

What is electricity?

When we refer to **electricity**, what we usually mean is **electric current**, which is the **flow of electric charge**. Electricity occurs naturally. For example, lightning, static electricity, bioelectricity produced in living things like electric eels and even in humans to deliver messages from the brain.




Electricity powers many of the things we use **everyday** - televisions, phones, computers, lights and microwaves. Over time, **scientists** worked out how to **generate electricity** so that it could be used **to make things work**. This meant that **electricity** was more **readily available** and **things** could be **powered** more **easily**. This sort of electricity is known as **current electricity**.

THINKING POINT:



What is electricity? Can you think of any natural examples?

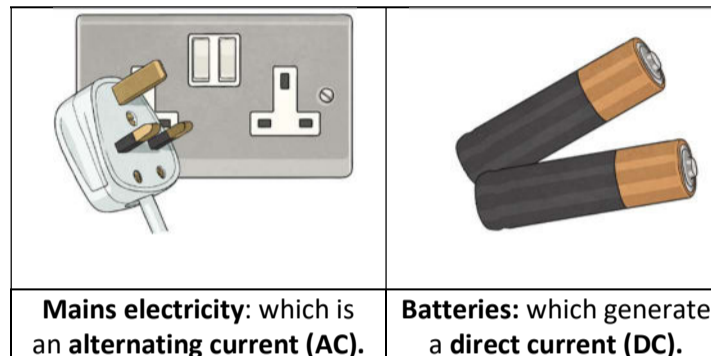Current electricity is a **flow** of **electrical charge** through a **material**. Often it **flows** through **wires** to **travel** from a **power source** to an **appliance**. There are **two types** of **electrical current** that we **use** to **power appliances**:




Where Does Electricity Come From?

An **energy source** is a way of **powering something**. **Electricity** is a **secondary energy source**.

Since **electricity** is a **secondary source of energy**, it needs to be **generated**, or made, from a **primary source of energy**.

Primary sources of energy include:

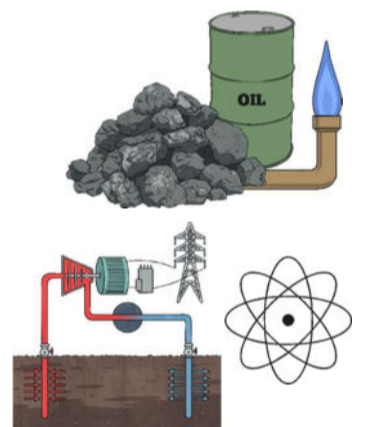- Burning fossil fuels like gas, oil or coal creates heat, which can be generated in to electricity.
- Harnessing wind power to turn windmills to generate electricity.
- Harnessing solar power to shine on special panels and turn UV energy in to electricity.
- Nuclear energy – combining or splitting atoms, which creates heat, which can be turned to electricity.



THINKING POINT:



Which of these is the most environmentally friendly?

Will we ever run out of electricity?

There are **several different ways** of **generating electricity** to use to **power appliances**.

Some of these **methods** of generating electricity are **renewable**. This means they will **never run out**, so we can use them to **generate electricity forever**.

However, **some methods are non-renewable**. This means that they **will run out**, and when they do we will not be able to use them to **generate electricity**.

Renewable	Non-renewable
Solar Nuclear Geothermal Hydro Wind	Fossil fuels *Oil *Coal *Natural gases



Coal, oil and natural gas will all **run out one day**. When they do, we will **not** be **able to burn** these materials to **generate electricity**. However, these materials are **cheaper** than the **non-renewable sources**. For this reason, **most** of our **electricity** is currently **generated** from **fossil fuels**.

THINKING POINT:



Will we ever run out of electricity? What will happen when the fossil fuels run out?

EXPLORE AND INVESTIGATE:

EXPLORE AND INVESTIGATE	
HYPOTHESISE ENQUIRE TEST RECORD REPORT CONCLUDE	<p><u>What would life be like without electricity?</u></p> <p>Look around you. Identify all of the electrical appliances.</p> <p>Sort these appliances in to groups whether they run by mains electricity or batteries.</p> <p>Discuss ways things would be different.</p> <p>What would your classroom be like?</p> <p>How would you learn?</p> <p>What would your home be like?</p> <p>How would people stay in touch?</p>

KEY ASSESSMENT AND APPLICATION OPPORTUNITIES:

EXS:

1. What is electricity? Can you explain it in 5 sentences?
2. Where does electricity come from?

GDS:

1. Will we ever run out of electricity?

UNDERSTAND, DESCRIBE AND EXPLAIN:

To recognise that a switch opens and closes a circuit and associate this with whether or not a lamp lights in a simple series circuit


To identify whether or not a lamp will light in a simple series circuit, based on whether or not the lamp is part of a complete loop with a battery

To construct a simple series electrical circuit, identifying and naming its basic parts, including cells, wires, bulbs, switches and buzzers

Learning links:
Year 6: Science Electricity
Year 4: DT Rockband stages

Electrical circuit	Power supply	Mains (AC)	Battery (DC)	Positive	Negative	Complete	Incomplete
Switches	Dimmer switch	Pull switch	Paddle switch	Push-button switch		Selector switch	Electrons


Electrical circuits:
Current electricity is the *flow* of *electrical charge* through *materials*.
A *complete circuit* must have a *power supply*. This *power supply* could be the *mains*, or it could be a *battery*.
For a *circuit* to be *complete*, there *must* be *wires connected* to *both* the *positive* and *negative* ends of the *power supply*. *Electricity* can *only flow* around a *complete circuit* that has *no gaps*.

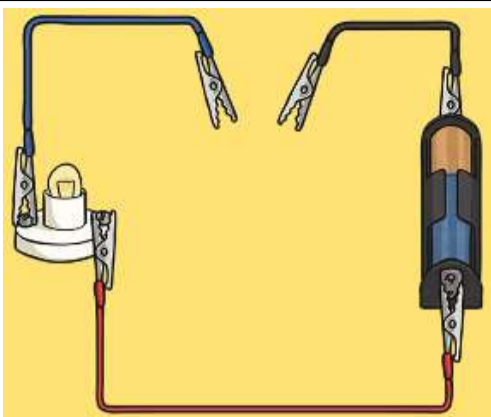

This is an <i>incomplete circuit</i> because: 1. There is a <i>gap</i> in the <i>circuit</i> , so the <i>electrical current cannot flow</i> around it. 2. The <i>wires do not connect</i> to <i>both</i> the <i>positive and negative ends</i> of the <i>power supply</i> (the battery).	This is a <i>complete circuit</i> because: 1. There is a <i>power supply</i> (the battery). 2. There are <i>no gaps</i> anywhere, so the electrical current can flow around the <i>entire circuit</i> . 3. The <i>wires connect</i> to both the <i>positive</i> and <i>negative ends</i> of the <i>battery</i> .

THINKING POINT:

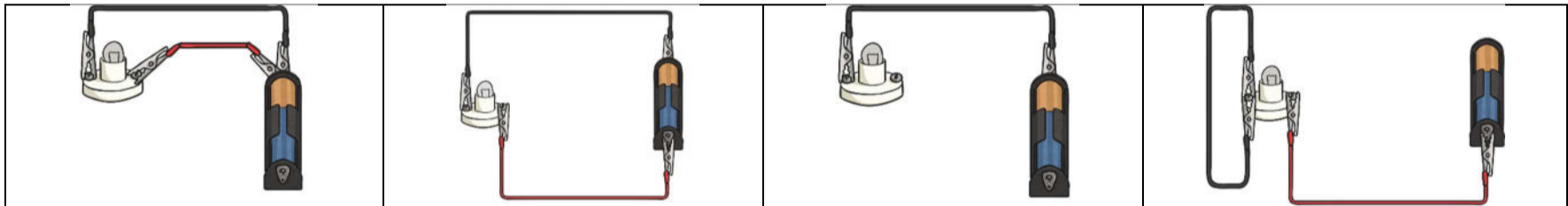Look at the circuits below. Are they complete or incomplete? Why?



The different parts of an electrical circuit:

Battery holder	Crocodile Clip	Battery (cell)	Bulb	Bulb holder	Motor	Buzzer	Wires


Building and controlling circuits:
Complete circuits must have a *power source* (mains or battery) which is *connected* at both ends (positive and negative) by *wires* made from an *electrical conductor* (i.e. metal). These *wires* must *connect* the *power source* to the *appliance* with no gaps.
If you successfully build a *complete circuit*, the *appliance* will *remain on* until the *circuit is broken*. This poses *problems* in *everyday life*, as we are *unable* to *control* the *electrical appliance*. Would you want the kettle to boil all day and the lights to be on endlessly?
This is where *switches* are used. There are *wide varieties* of *switches* useful for *different purposes*:




Dimmer switch	Pull switch	Paddle switch	Push-button switch	Selector switch

THINKING POINT:

Why have humans designed different switches like the ones above?

How does a switch work?
A *switch* '*breaks*' a *complete circuit* on *purpose* to *stop the flow* of *electrons* when it is *off*.
When the *switch* is *on*, the *circuit* is *complete* and so the *electrons* are able to *flow* around the *circuit*.
A *circuit with a switch* is not the same as an *incomplete circuit*. In an *incomplete circuit*, the *electrons* are *unable* to *flow* at all *whether the switch is on or off*.

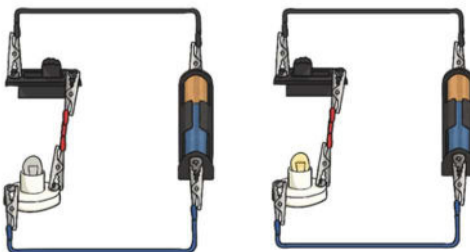

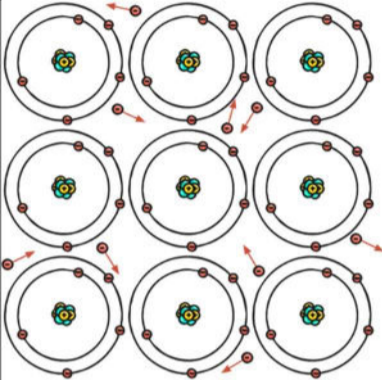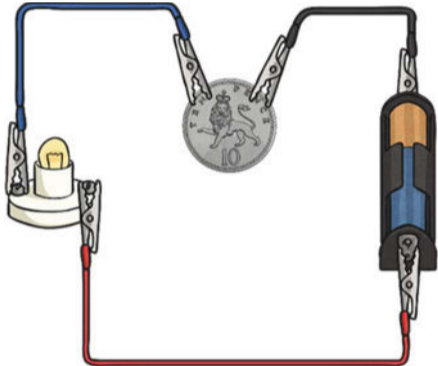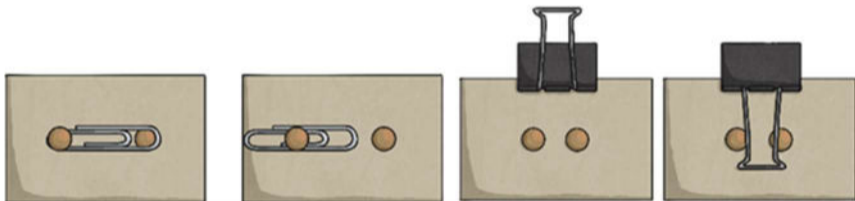UNDERSTAND, DESCRIBE AND EXPLAIN:								
To recognise some common conductors and insulators, and associate metals with being good conductors	Conductors	Insulators	Atoms	Electrons	Electric current	Electric flow	Complete	Incomplete
	Materials	Testing	Conductivity	Insulation	Metals	Wood	Plastic	Glass
	<p>Electrical conductors and insulators: A conductor of electricity is a material that electricity can flow through easily. Metals are good conductors. An insulator of electricity is a material which electricity is unable to flow through. Wood, plastic and glass are good insulators.</p> <p>Electrical insulators, such as woods, plastics and glass: In most materials, the atoms are organised like this: The electrons cannot move freely in these materials and therefore no electric current can flow through. These materials are called electrical insulators. If you create a circuit which includes an electrical insulator, it will be incomplete (even if it looks complete!) as no electrons will flow through the material.</p>							
Learning links: Year 6: Science Electricity Year 4: DT Rockband stages				<p>THINKING POINT:</p> <p>Can you think of some everyday items where insulation is useful?</p>			<p>Electrical</p> <p>conductors, such as metal: In some materials, some of the electrons are free electrons and can move. If you create a circuit with these materials, the free electrons can be made to move in one direction, creating an electric current. These materials are called electrical conductors.</p>	
				<p>THINKING POINT:</p> <p>Can you think of some everyday items where conduction is useful?</p>				
<p>Testing for conductivity: You can test whether a material is a conductor or an insulator by setting up a complete circuit and then adding a material to the circuit using an extra pair of wires. If the circuit continues to work with the material in the circuit, this shows good conductivity. However, if the circuit becomes incomplete when the material is added, this shows that this material is a poor conductor and therefore an insulator.</p>								
				<p>THINKING POINT:</p> <p>Would you be able to set up this simple investigation? Which materials would you test?</p>				
EXPLORE AND INVESTIGATE:								
HYPOTHESISE ENQUIRE TEST RECORD REPORT CONCLUDE	<p>Investigating conductivity and switches:</p> <ol style="list-style-type: none">Build a complete circuit with at least a battery and an appliance (bulb/buzzer/motor).Add in 2 extra wires with crocodile clips and test the conductivity of different materials. Record which materials were successful or not.How does the brightness of the bulb change with the different materials? Are some materials better than other conductors?Sticking two pins in to a piece of cardboard create 2 switches as shown in the images below.Test the switches in the different positions.Time how long it takes to break and reconnect the circuit. Does it change for different switches?							
								
KEY ASSESSMENT AND APPLICATION OPPORTUNITIES:								
<p>EXS:</p> <ol style="list-style-type: none">What are the least amount of components needed to create a working circuit with a bulb?Can you build a complete, simple, series circuit with a switch to control a bulb/buzzer?What is the difference between a conductor and an insulator?				<p>GDS:</p> <ol style="list-style-type: none">Can you build a complete, simple series circuit and investigate what happens when you add more or less of a component and explain your findings?Why do you think wires made of copper and coated in plastic?				